

Sequential Logic

CSIM601251

Instructor: Tim Dosen DDAK

Slide By : Erdefi Rakun

Fasilkom UI




Outline

- Memory Elements
- Latches: *S-R* Latch, *D* Latch
- Flip-flops: *S-R* flip-flop, *D* flip-flop, *J-K* flip-flops, *T* flip-flops
- Asynchronous Inputs
- Synchronous Sequential Circuit Analysis

Note: These slides are taken from Aaron Tan's slide


Introduction (1/2)

 - Two classes of logic circuits
 - Combinational
 - Sequential
- **Combinational Circuit**
 - Each output depends entirely on the immediate (present) inputs.



■ Sequential Circuit

 - Each output depends on both present inputs and state.



Introduction (2/2)

- Two types of sequential circuits:
 - **Synchronous**: outputs change only at specific time
 - **Asynchronous**: outputs change at any time
- Multivibrator: a class of sequential circuits
 - Bistable (2 stable states)
 - Monostable or one-shot (1 stable state)
 - Astable (no stable state)
- Bistable logic devices
 - **Latches** and **flip-flops**.
 - They differ in the methods used for changing their state.

Memory Elements (1/3)

- **Memory element:** a device which can remember value indefinitely, or change value on command from its inputs.



■ Characteristic table:


Command (at time t)	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1

$Q(t)$ or Q : current state


$Q(t+1)$ or Q^+ : next state

Memory Elements (2/3)

- Memory element with clock.

 


- Clock is usually a square wave.

 

Memory Elements (3/3)

 - Two types of triggering/activation
 - Pulse-triggered
 - Edge-triggered
- Pulse-triggered
 - Latches
 - ON = 1, OFF = 0
- Edge-triggered
 - Flip-flops
 - Positive edge-triggered (ON = from 0 to 1; OFF = other time)
 - Negative edge-triggered (ON = from 1 to 0; OFF = other time)



Outline

- Memory Elements
- Latches: *S-R* Latch, *D* Latch
- Flip-flops: *S-R* flip-flop, *D* flip-flop, *J-K* flip-flops, *T* flip-flops
- Asynchronous Inputs
- Synchronous Sequential Circuit Analysis


Note: These slides are taken from Aaron Tan's slide

S-R Latch (1/3)


- Two inputs: S and R .
- Two complementary outputs: Q and Q' .
 - When $Q = \text{HIGH}$, we say latch is in SET state.
 - When $Q = \text{LOW}$, we say latch is in RESET state.
- For active-high input S - R latch (also known as NOR gate latch)
 - $R = \text{HIGH}$ and $S = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
 - $S = \text{HIGH}$ and $R = \text{LOW} \rightarrow Q$ becomes HIGH (SET state)
 - Both R and S are LOW \rightarrow No change in output Q
 - Both R and S are HIGH \rightarrow Outputs Q and Q' are both LOW (invalid!)
- Drawback: invalid condition exists and must be avoided.

S-R Latch (2/3)

- Active-high input S-R latch:

 


- Block diagram:

 

S-R Latch (3/3)

 - Characteristic table for active-high input S-R latch:




<i>S</i>	<i>R</i>	<i>Q</i>	<i>Q'</i>	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

<i>S</i>	<i>R</i>	<i>Q(t+1)</i>	
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	indeterminate	

Q(t+1) = ?

Gated S-R Latch

 
- S-R latch + *enable input* (EN) and 2 NAND gates → a gated S-R latch.



- Outputs change (if necessary) only when *EN* is high.

Gated *D* Latch (1/2)

 - Make input R equal to S' \rightarrow gated *D* latch.
- *D* latch eliminates the undesirable condition of invalid state in the *S-R* latch.



Gated *D* Latch (2/2)

- When *EN* is high,
 - *D* = HIGH → latch is SET
 - *D* = LOW → latch is RESET
- Hence when *EN* is high, *Q* “follows” the *D* (data) input.
- Characteristic table:

<i>EN</i>	<i>D</i>	<i>Q</i> (<i>t</i> +1)	
1	0	0	Reset
1	1	1	Set
0	X	<i>Q</i> (<i>t</i>)	No change

When *EN*=1, *Q*(*t*+1) = ?


Outline

- Memory Elements
- Latches: S - R Latch, D Latch
- Flip-flops: S - R flip-flop, D flip-flop, J - K flip-flops, T flip-flops
- Asynchronous Inputs
- Synchronous Sequential Circuit Analysis

Note: These slides are taken from Aaron Tan's slide


Flip-Flops (1/2)

 - Flip-flops are synchronous bistable devices.
- Output changes state at a specified point on a triggering input called the **clock**.
- Change state either at the positive (rising) edge, or at the negative (falling) edge of the clock signal.




Flip-Flops (2/2)

 - *S-R flip-flop*, *D flip-flop*, and *J-K flip-flop*.
- Note the “>” symbol at the clock input.




Positive edge-triggered flip-flops

 

Negative edge-triggered flip-flops

S-R Flip-Flop

 - **S-R flip-flop**: On the triggering edge of the clock pulse,
 - $R = \text{HIGH}$ and $S = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
 - $S = \text{HIGH}$ and $R = \text{LOW} \rightarrow Q$ becomes HIGH (SET state)
 - Both R and S are LOW \rightarrow No change in output Q
 - Both R and S are HIGH \rightarrow Invalid!
- **Characteristic table** of positive edge-triggered S-R flip-flop:




S	R	CLK	$Q(t+1)$	Comments
0	0	X	$Q(t)$	No change
0	1	\uparrow	0	Reset
1	0	\uparrow	1	Set
1	1	\uparrow	?	Invalid

X = irrelevant ("don't care")

\uparrow = clock transition LOW to HIGH

D Flip-Flop (1/2)

 - **D flip-flop**: Single input D (data). On the triggering edge of the clock pulse,
 - $D = \text{HIGH} \rightarrow Q$ becomes HIGH (SET state)
 - $D = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
- Hence, Q “follows” D at the clock edge.
- Convert S - R flip-flop into a D flip-flop: add an inverter.




A positive edge-triggered D flip-flop formed with an S - R flip-flop.

D	CLK	$Q(t+1)$	Comments
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH

D Flip-Flop (2/2)

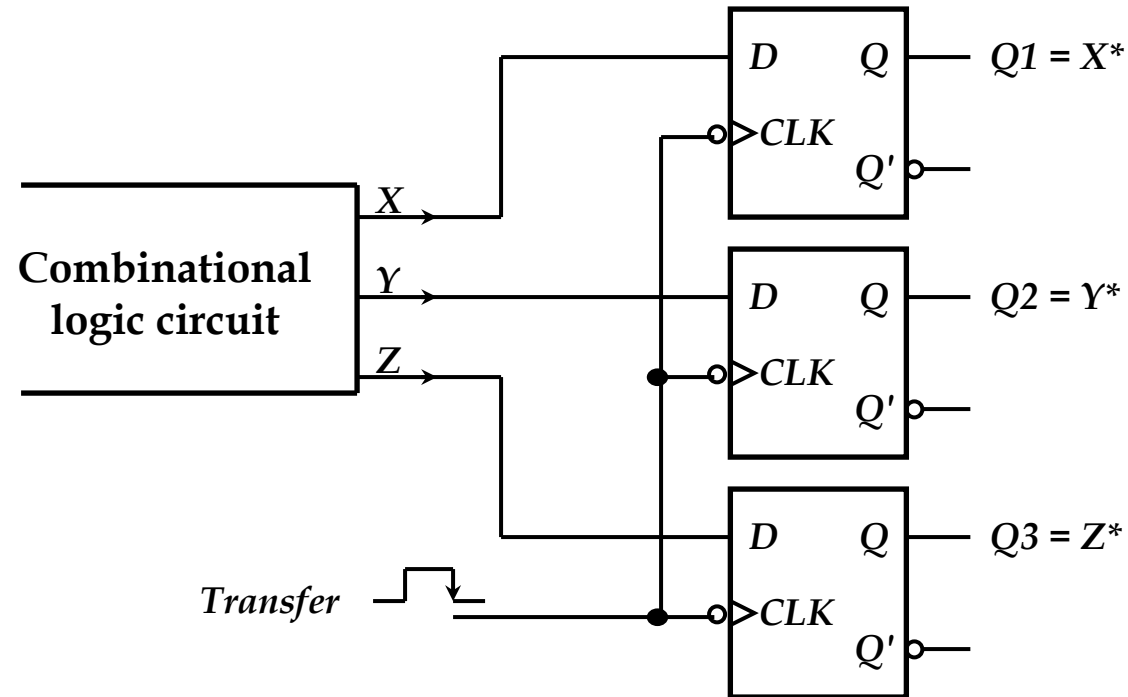- Application: Parallel data transfer.
 - To transfer logic-circuit outputs X , Y , Z to flip-flops $Q1$, $Q2$ and $Q3$ for storage.




* After occurrence of negative-going transition

J-K Flip-Flop (1/2)

- *J-K flip-flop*: Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a toggle state
 - $J = \text{HIGH}$ and $K = \text{LOW} \rightarrow Q$ becomes HIGH (SET state)
 - $K = \text{HIGH}$ and $J = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
 - Both J and K are LOW \rightarrow No change in output Q
 - Both J and K are HIGH \rightarrow Toggle

J-K Flip-Flop (2/2)

- J-K flip-flop circuit:

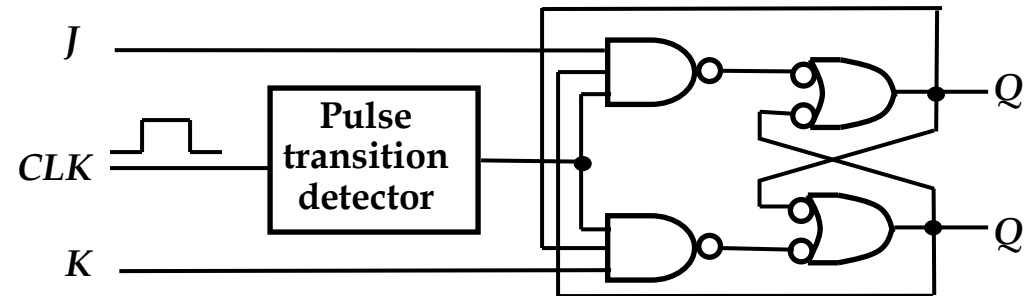

- Characteristic table:


J	K	CLK	$Q(t+1)$	Comments
0	0	\uparrow	$Q(t)$	No change
0	1	\uparrow	0	Reset
1	0	\uparrow	1	Set
1	1	\uparrow	$Q(t)'$	Toggle

$$Q(t+1) = ?$$

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

T Flip-Flop

 - *T* flip-flop: Single input version of the *J-K* flip-flop, formed by tying both inputs together.



■ Characteristic table:


<i>T</i>	<i>CLK</i>	<i>Q(t+1)</i>	Comments
0	↑	<i>Q(t)</i>	No change
1	↑	<i>Q(t)'</i>	Toggle

$$Q(t+1) = ?$$

<i>Q</i>	<i>T</i>	<i>Q(t+1)</i>
0	0	0
0	1	1
1	0	1
1	1	0


Flip-flop Behavior Example

 - Use the characteristic tables to find the output waveforms for the flip-flops shown:



Flip-Flop Behavior Example (continued)

 - Use the characteristic tables to find the output waveforms for the flip-flops shown:



Outline

- Memory Elements
- Latches: S - R Latch, D Latch
- Flip-flops: S - R flip-flop, D flip-flop, J - K flip-flops, T flip-flops
- Asynchronous Inputs
- Synchronous Sequential Circuit Analysis



Note: These slides are taken from Aaron Tan's slide

Asynchronous Inputs (1/2)

- S - R , D and J - K inputs are **synchronous inputs**, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock; example: *preset* (PRE) and *clear* (CLR) [or *direct set* (SD) and *direct reset* (RD)].
- When PRE =HIGH, Q is immediately set to HIGH.
- When CLR =HIGH, Q is immediately cleared to LOW.
- Flip-flop in normal operation mode when both PRE and CLR are LOW.

Asynchronous Inputs (2/2)

 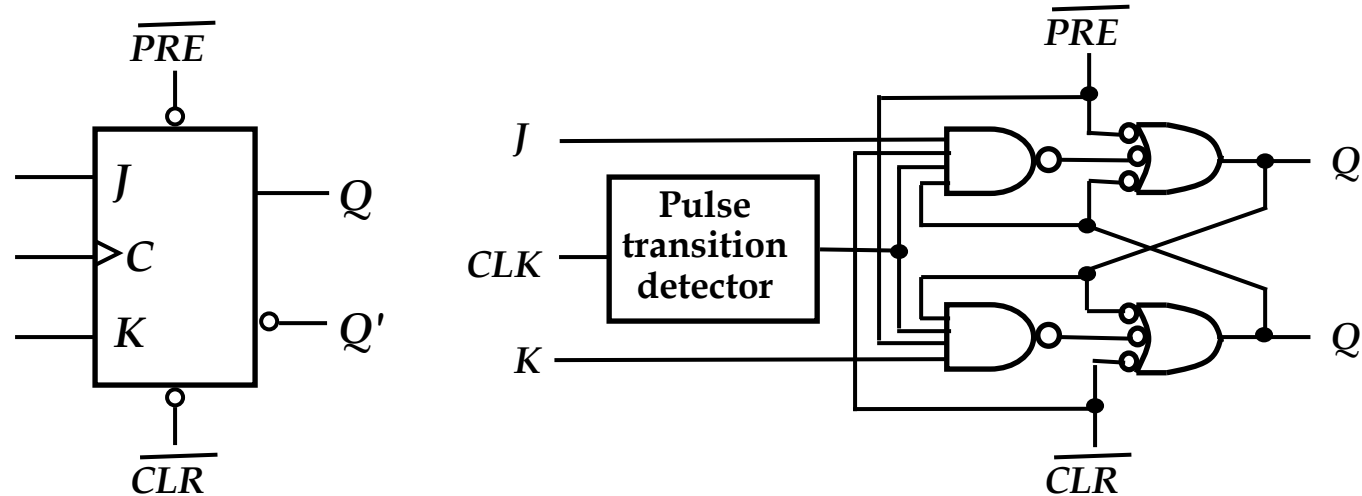- A J-K flip-flop with active-low PRESET and CLEAR asynchronous inputs.



Outline

- Memory Elements
- Latches: S - R Latch, D Latch
- Flip-flops: S - R flip-flop, D flip-flop, J - K flip-flops, T flip-flops
- Asynchronous Inputs
- Synchronous Sequential Circuit Analysis

Note: These slides are taken from Aaron Tan's slide

Synchronous Sequential Circuits

- Building blocks: logic gates and flip-flops.
- Flip-flops make up the memory while the gates form one or more combinational subcircuits.
- We have discussed *S-R* flip-flop, *J-K* flip-flop, *D* flip-flop and *T* flip-flop.

Flip-Flop Characteristic Tables

- Each type of flip-flop has its own behaviour, shown by its **characteristic table**.

J	K	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

S	R	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

D	$Q(t+1)$
0	0 Reset
1	1 Set

T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q(t)'$ Toggle

Sequential Circuits: Analysis (1/7)

- Given a sequential circuit diagram, we can analyze its behaviour by deriving its *state table* and hence its *state diagram*.
- Requires *state equations* to be derived for the flip-flop inputs, as well as *output functions* for the circuit outputs other than the flip-flops (if any).
- We use $A(t)$ and $A(t+1)$ (or simply A and A^+) to represent the present state and next state, respectively, of a flip-flop represented by A .

Sequential Circuits: Analysis (2/7)

- Example using D flip-flops

State equations:

$$A^+ = A \cdot x + B \cdot x$$

$$B^+ = A' \cdot x$$

Output function:

$$y = (A + B) \cdot x'$$

 


Figure 1

Sequential Circuits: Analysis (3/7)

- From the *state equations* and *output function*, we derive the *state table*, consisting of all possible binary combinations of present states and inputs.
- State table
 - Similar to truth table.
 - Inputs and present state on the left side.
 - Outputs and next state on the right side.
- m flip-flops and n inputs $\rightarrow 2^{m+n}$ rows.

Sequential Circuits: Analysis (4/7)

- *State table* for circuit of Figure 1:

State equations:

$$A^+ = A \cdot x + B \cdot x$$

$$B^+ = A' \cdot x$$

Output function:

$$y = (A + B) \cdot x'$$

Present State		Input x	Next State		Output y
A	B		A^+	B^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Sequential Circuits: Analysis (5/7)

- Alternative form of state table:

Full table

Present State		Input x	Next State		Output y
A	B		A^+	B^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Compact table

Present State AB	Next State		Output	
	$x=0$ A^+B^+	$x=1$ A^+B^+	$x=0$ y	$x=1$ y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

Sequential Circuits: Analysis (6/7)



- From the *state table*, we can draw the *state diagram*.
- State diagram
 - Each state is denoted by a circle.
 - Each arrow (between two circles) denotes a transition of the sequential circuit (a row in state table).
 - A label of the form a/b is attached to each arrow where a (if there is one) denotes the inputs while b (if there is one) denotes the outputs of the circuit in that transition.
- Each combination of the flip-flop values represents a state. Hence, m flip-flops \rightarrow up to 2^m states.

Sequential Circuits: Analysis (7/7)

- **State diagram** of the circuit of Figure 1:

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
AB	A^+B^+	A^+B^+	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

DONE!

  


Flip-Flop Input Function (1/3)

- The outputs of a sequential circuit are functions of the present states of the flip-flops and the inputs. These are described algebraically by the *circuit output functions*.
 - In Figure 1: $y = (A + B) \cdot x'$
- The part of the circuit that generates inputs to the flip-flops are described algebraically by the *flip-flop input functions* (or *flip-flop input equations*).
- The flip-flop input functions determine the next state generation.
- From the flip-flop input functions and the characteristic tables of the flip-flops, we obtain the next states of the flip-flops.

Flip-Flop Input Function (2/3)

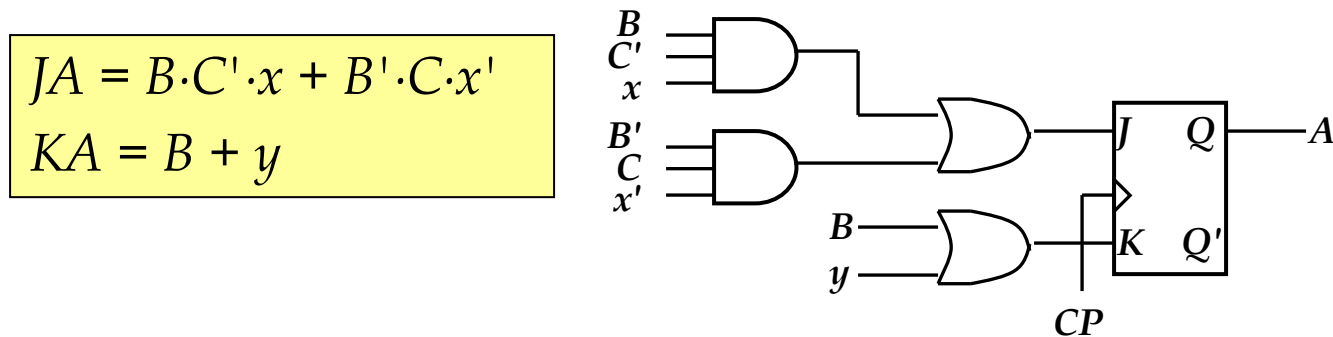- Example: circuit with a JK flip-flop.
- We use 2 letters to denote each flip-flop input: the first letter denotes the input of the flip-flop (J or K for J - K flip-flop, S or R for S - R flip-flop, D for D flip-flop, T for T flip-flop) and the second letter denotes the name of the flip-flop.



Flip-Flop Input Function (3/3)

- In Figure 1, we obtain the following state equations by observing that $Q^+ = DQ$ for a D flip-flop:

$$A^+ = A \cdot x + B \cdot x \quad (\text{since } DA = A \cdot x + B \cdot x)$$

$$B^+ = A' \cdot x \quad (\text{since } DB = A' \cdot x)$$


 


Figure 1

Analysis: Example #2 (1/3)

 - Given Figure 2, a sequential circuit with two J - K flip-flops A and B , and one input x .



- Obtain the flip-flop input functions from the circuit:

$$JA = B$$

$$JB = x'$$

$$KA = B \cdot x'$$

$$KB = A' \cdot x + A \cdot x' = A \oplus x$$

Analysis: Example #2 (2/3)

$$JA = B$$

$$JB = x'$$

$$KA = B \cdot x'$$

$$KB = A' \cdot x + A \cdot x' = A \oplus x$$

- Fill the state table using the above functions, knowing the characteristics of the flip-flops used.

<i>J</i>	<i>K</i>	<i>Q(t+1)</i>	Comments
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q(t)'</i>	Toggle

Present state		Input	Next state		Flip-flop inputs			
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i> ⁺	<i>B</i> ⁺	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	0	1	1	1	1	0
0	1	1	0	1	1	0	0	1
1	0	0	1	0	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	1	1	1	1	1	1
1	1	1	1	1	1	0	0	0

Analysis: Example #2 (3/3)

- Draw the state diagram from the state table.

Present state		Input x	Next state		Flip-flop inputs			
A	B		A^+	B^+	J_A	K_A	J_B	K_B
0	0	0			0	0	1	0
0	0	1			0	0	0	1
0	1	0			1	1	1	0
0	1	1			1	0	0	1
1	0	0			0	0	1	1
1	0	1			0	0	0	0
1	1	0			1	1	1	1
1	1	1			1	0	0	0



Analysis: Example #3 (1/3)

- Derive the state table and state diagram of this circuit.

 


Figure 3

- Flip-flop input functions:

$$JA = B$$

$$KA = B'$$

$$JB = KB = (A \oplus x)' = A \cdot x + A' \cdot x'$$

Analysis: Example #3 (2/3)

- Flip-flop input functions:

$$JA = B$$

$$JB = KB = (A \oplus x)' = A \cdot x + A' \cdot x'$$

$$KA = B'$$


- State table:

Present state		Input x	Next state		Output y	Flip-flop inputs			
A	B		A^+	B^+		JA	KA	JB	KE
0	0	0			0	0	1	1	1
0	0	1			1	0	1	0	0
0	1	0			1	1	0	1	1
0	1	1			0	1	0	0	0
1	0	0			1	0	1	0	0
1	0	1			0	0	1	1	1
1	1	0			0	1	0	0	0
1	1	1			1	1	0	1	1

Analysis: Example #3 (3/3)

- State diagram:

Present state		Input x	Next state		Output y	Flip-flop inputs			
A	B		A^+	B^+		JA	KA	JB	KB
0	0	0			0	0	1	1	1
0	0	1			1	0	1	0	0
0	1	0			1	1	0	1	1
0	1	1			0	1	0	0	0
1	0	0			1	0	1	0	0
1	0	1			0	0	1	1	1
1	1	0			0	1	0	0	0
1	1	1			1	1	0	1	1

 

Flip-Flop Excitation Tables (1/2)

- *Analysis*: Starting from a circuit diagram, derive the state table or state diagram.
- *Design*: Starting from a set of specifications (in the form of state equations, state table, or state diagram), derive the logic circuit.
- *Characteristic tables* are used in analysis.
- *Excitation tables* are used in design.

Flip-Flop Excitation Tables (2/2)

- Excitation tables*: given the required transition from present state to next state, determine the flip-flop input(s).

Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR Flip-flop

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-flop

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0


T Flip-flop

Sequential Circuits: Design

- Design procedure:
 - Start with circuit specifications – description of circuit behaviour, usually a state diagram or state table.
 - Derive the state table.
 - Perform state reduction if necessary.
 - Perform state assignment.
 - Determine number of flip-flops and label them.
 - Choose the type of flip-flop to be used.
 - Derive circuit excitation and output tables from the state table.
 - Derive circuit output functions and flip-flop input functions.
 - Draw the logic diagram.

Design: Example #1 (1/5)

 - Given the following state diagram, design the sequential circuit using *JK* flip-flops.




Questions:

How many flip-flops are needed?

How many input variable are there?


Design: Example #1 (2/5)

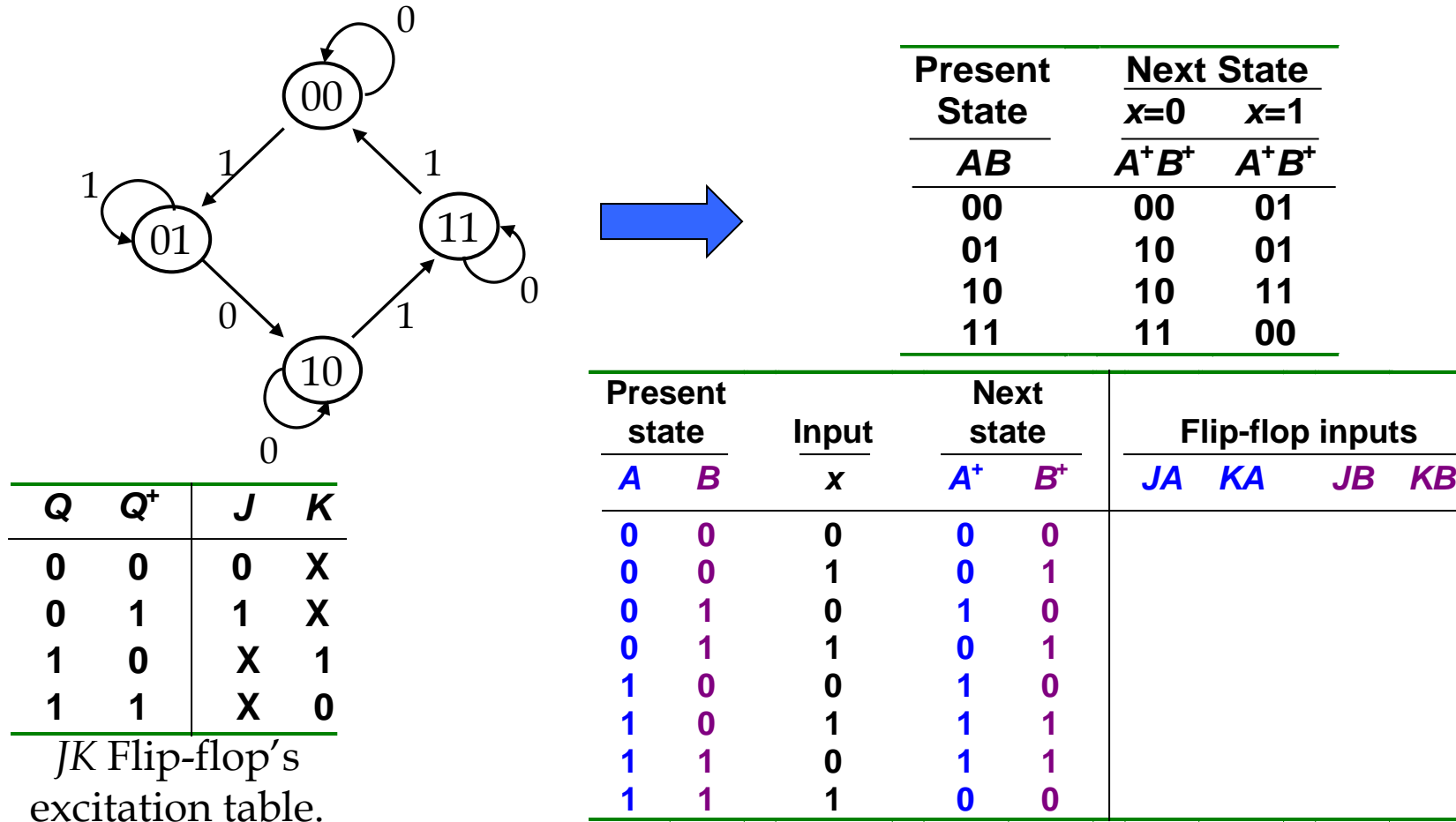- Circuit state/excitation table, using JK flip-flops.



Design: Example #1 (3/5)

- Block diagram.

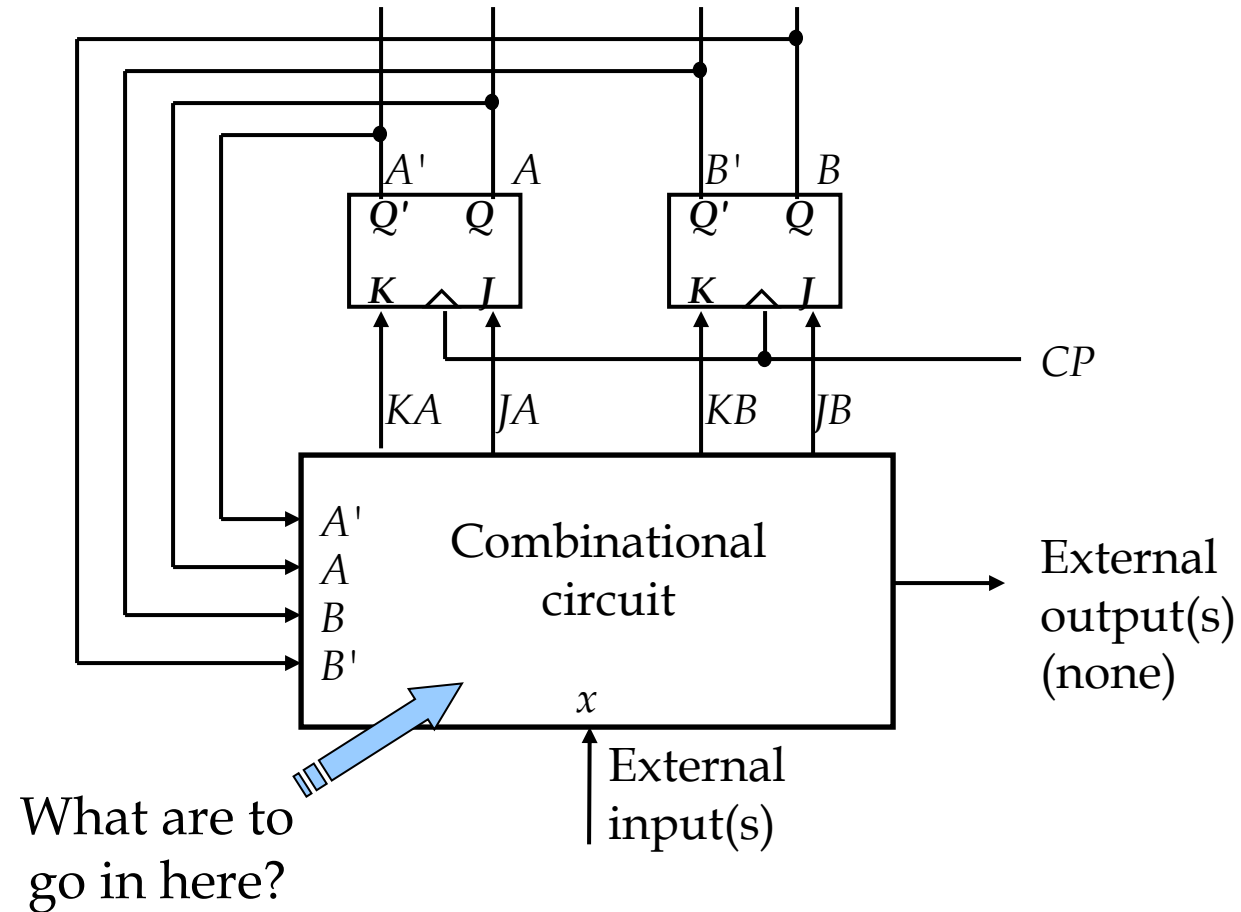

Design: Example #1 (4/5)

- From state table, get flip-flop input functions.

Present state		Input x	Next state		Flip-flop inputs			
A	B		A^+	B^+	JA	KA	JB	KB
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

		B			
$A \backslash Bx$		00	01	11	10
	0		1	X	X
A	1		1	X	X

$JB = x$

		B			
$A \backslash Bx$		00	01	11	10
	0	X	X		1
A	1	X	X	1	

$KB = (A \oplus x)'$

		B			
$A \backslash Bx$		00	01	11	10
	0				1
A	1	X	X	X	X

$JA = B \cdot x'$

		B			
$A \backslash Bx$		00	01	11	10
	0	X	X	X	X
A	1			1	

$KA = B \cdot x$

Design: Example #1 (5/5)

- Flip-flop input functions:


$$JA = B \cdot x'$$

$$JB = x$$

$$KA = B \cdot x$$

$$KB = (A \oplus x)'$$

- Logic diagram:

 

Design: Example #2 (1/3)

- Using D flip-flops, design the circuit based on the state table below. (Exercise: Design it using JK flip-flops.)

Present state		Input	Next state		Output
A	B		A^+	B^+	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

Design: Example #2 (2/3)

- Determine expressions for flip-flop inputs and the circuit output y .

Present state		Input x	Next state		Output y
A	B		A^+	B^+	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

$$DA(A,B,x) = \sum m(2,4,5,6)$$

$$DB(A,B,x) = \sum m(1,3,5,6)$$

$$y(A,B,x) = \sum m(1,5)$$

		Bx			
		00	01	11	10
A	0				1
	1	1	1		1

x

$$DA = A \cdot B' + B \cdot x'$$

		Bx			
		00	01	11	10
A	0		1	1	
	1		1		1

x

$$DB = A' \cdot x + B' \cdot x + A \cdot B \cdot x'$$

		Bx			
		00	01	11	10
A	0		1		
	1		1		

x

$$y = B' \cdot x$$


Design: Example #2 (3/3)

- From derived expressions, draw logic diagram:

$$DA = A \cdot B' + B \cdot x'$$

$$DB = A' \cdot x + B' \cdot x + A \cdot B \cdot x'$$

$$y = B' \cdot x$$

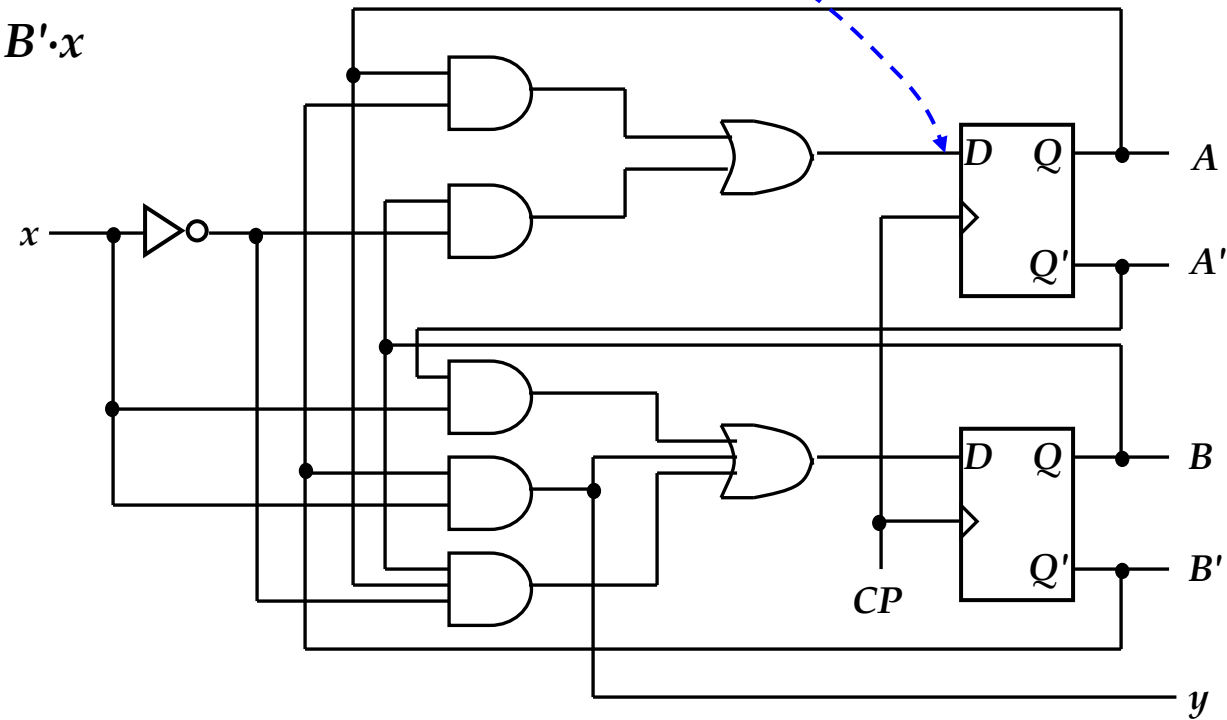

Design: Example #3 (1/4)

- Design involving unused states.

Present state			Input	Next state			Flip-flop inputs						Output
A	B	C		A ⁺	B ⁺	C ⁺	SA	RA	SB	RB	SC	RC	
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1

Given these

Derive these

Are there other unused states?

Unused state 000:

0	0	0	0	X	X	X	X	X	X	X	X	X	X
0	0	0	1	X	X	X	X	X	X	X	X	X	X

Design: Example #3 (2/4)

- From state table, obtain expressions for flip-flop inputs.

$SA = ?$

		C			
		00	01	11	10
A	00	X	X		
	01		1	1	
	11	X	X	X	X
	10	X	X	X	
		x			

$RA = ?$

		C			
		00	01	11	10
A	00	X	X	X	X
	01	X			X
	11	X	X	X	X
	10				1
		x			

$SB = ?$



		C			
		00	01	11	10
A	00	X	X	1	
	01	X			
	11	X	X	X	X
	10				
		x			

$RB = ?$

		C			
		00	01	11	10
A	00	X	X		X
	01		1	1	1
	11	X	X	X	X
	10	X	X	X	X
		x			

Design: Example #3 (3/4)

  - From state table, obtain expressions for flip-flop inputs (cont'd).



Design: Example #3 (4/4)

- From derived expressions, draw the logic diagram:

$$SA = B \cdot x$$

$$RA = C \cdot x'$$

$$SB = A' \cdot B' \cdot x$$

$$RB = B \cdot C + B \cdot x$$

$$SC = x'$$

$$RC = x$$

$$y = A \cdot x$$

