

Registers and Memory

CSIM601251

Instructor: Tim Dosen DDAK

Slide By : Erdefi Rakun

Fasilkom UI



Outline

- Register
- Memory
- Memory Unit
- Read/Write Operations
- Memory Arrays

Note: These slides are taken from Aaron Tan's slide

Registers

- N-bit register:
 - N flip-flops, possibly with added combinational gates that perform data-processing task
 - Capable of storing n bits of binary information
- Counter:
 - A register that goes through a predetermined sequence of states upon the application of clock pulse
- Register and Counter are sequential functional blocks that are used extensively in the design of digital systems

D Flip-Flops Register

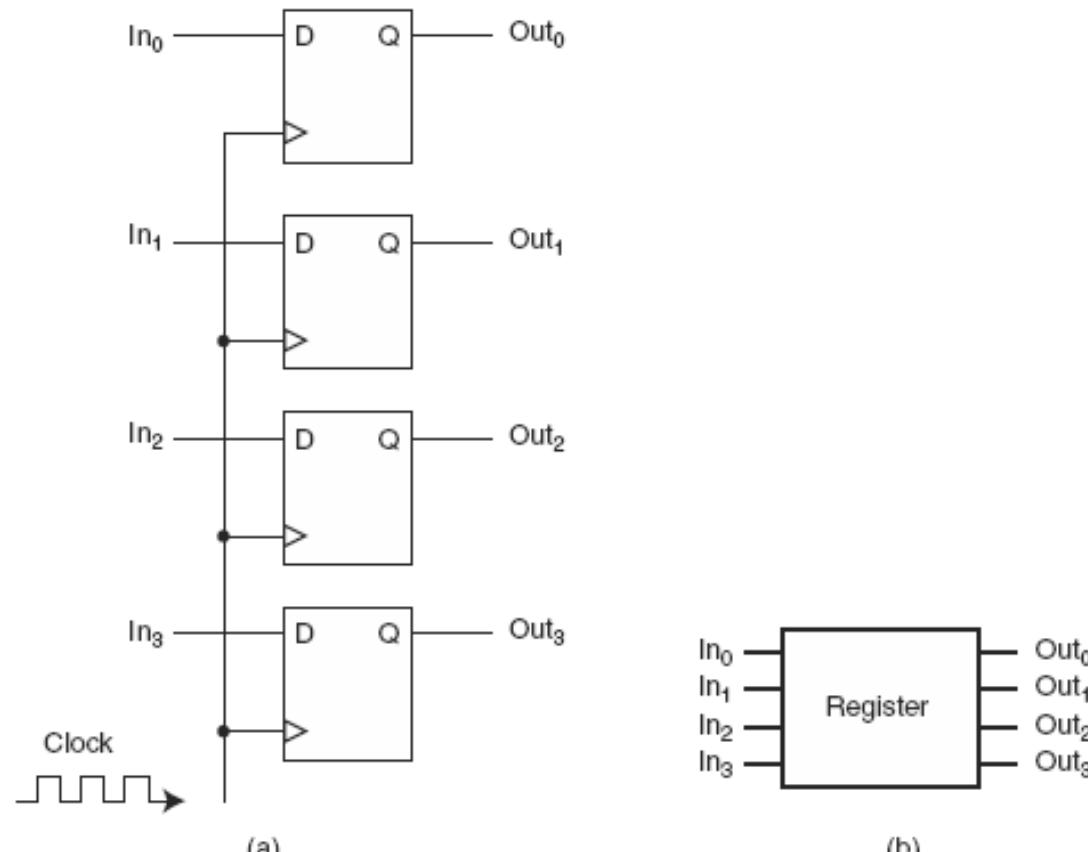


FIGURE 3.23 a) A 4-Bit Register
b) A Block Diagram for a 4-Bit Register

Binary Counters

- Counters are sequential circuits that cycle through some states.
- They can be implemented using flip-flops.
- 0000, 0001, 0010, 0011.....
 - Lower bit is complemented each time
 - Whenever it changes state from 1 to 0, the bit to the left is complemented
 - Each of the other bits changes state from 0 to 1 when all bit to the right are equal to 1

JK Flip-Flops Counter

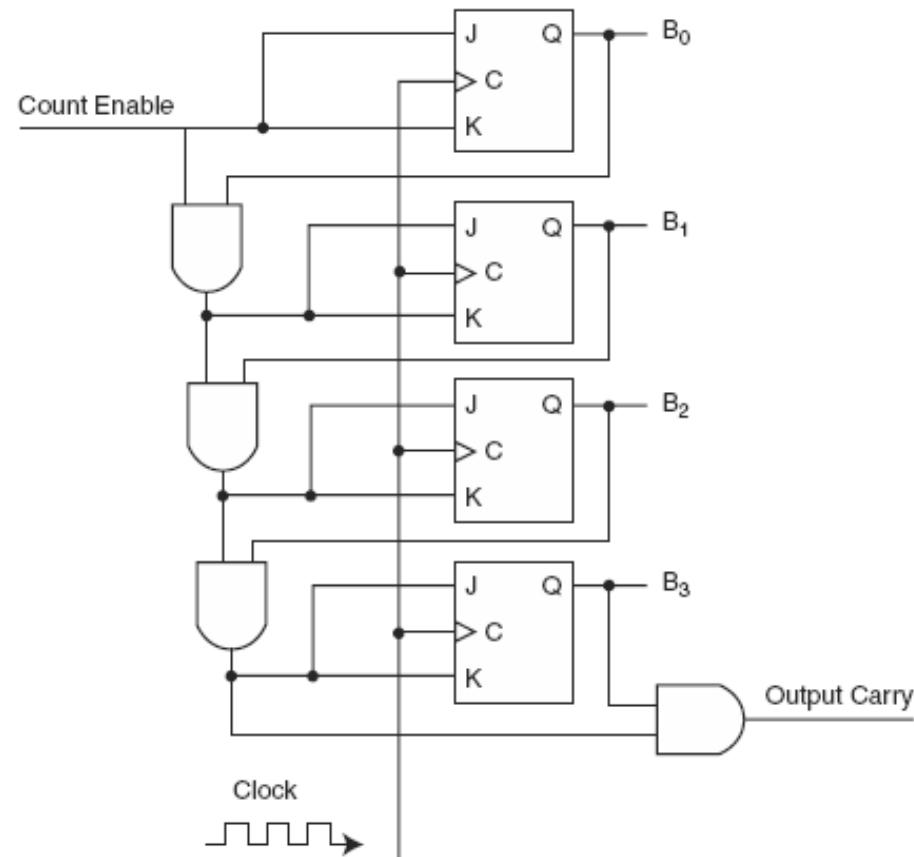


FIGURE 3.24 A 4-Bit Synchronous Counter Using JK Flip-Flops

Outline

- Register
- Memory
- Memory Unit
- Read/Write Operations
- Memory Arrays


Note: These slides are taken from Aaron Tan's slide

Memory (1/4)

- Memory stores programs and data.
- Definitions:
 - 1 byte = 8 bits
 - 1 word: in multiple of bytes, a unit of transfer between main memory and registers, usually size of register.
 - 1 KB (kilo-bytes) = 2^{10} bytes; 1 MB (mega-bytes) = 2^{20} bytes; 1 GB (giga-bytes) = 2^{30} bytes; 1 TB (tera-bytes) = 2^{40} bytes.
- Desirable properties: fast access, large capacity, economical cost, non-volatile.
- However, most memory devices do not possess all these properties.


Memory (2/4)

- Memory hierarchy

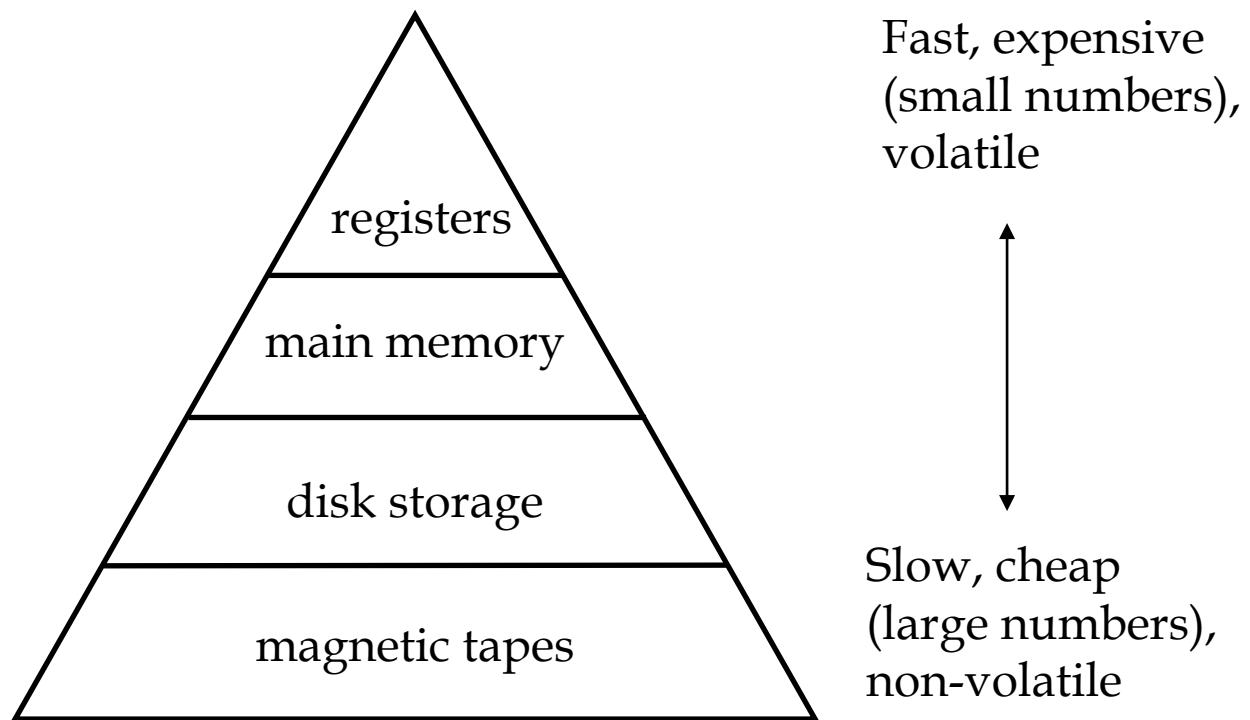

Memory (3/4)

- Data transfer

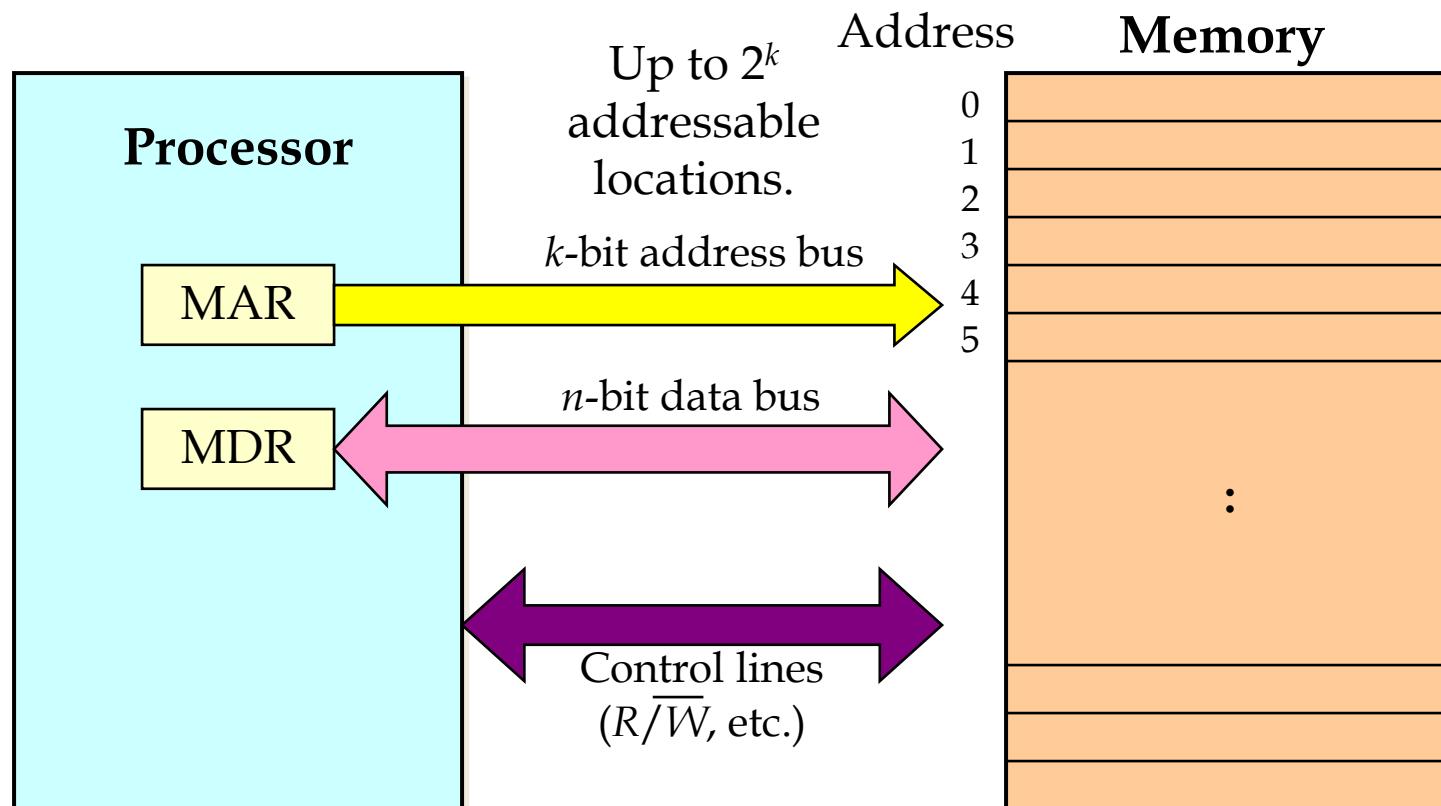


Memory (4/4)

- A memory unit stores binary information in groups of bits called *words*.
- The data consists of n lines (for n -bit words). Data input lines provide the information to be stored (*written*) into the memory, while data output lines carry the information out (*read*) from the memory.
- The address consists of k lines which specify which word (among the 2^k words available) to be selected for reading or writing.
- The control lines *Read* and *Write* (usually combined into a single control line *Read/Write*) specifies the direction of transfer of the data.

Memory Unit

- Block diagram of a memory unit:

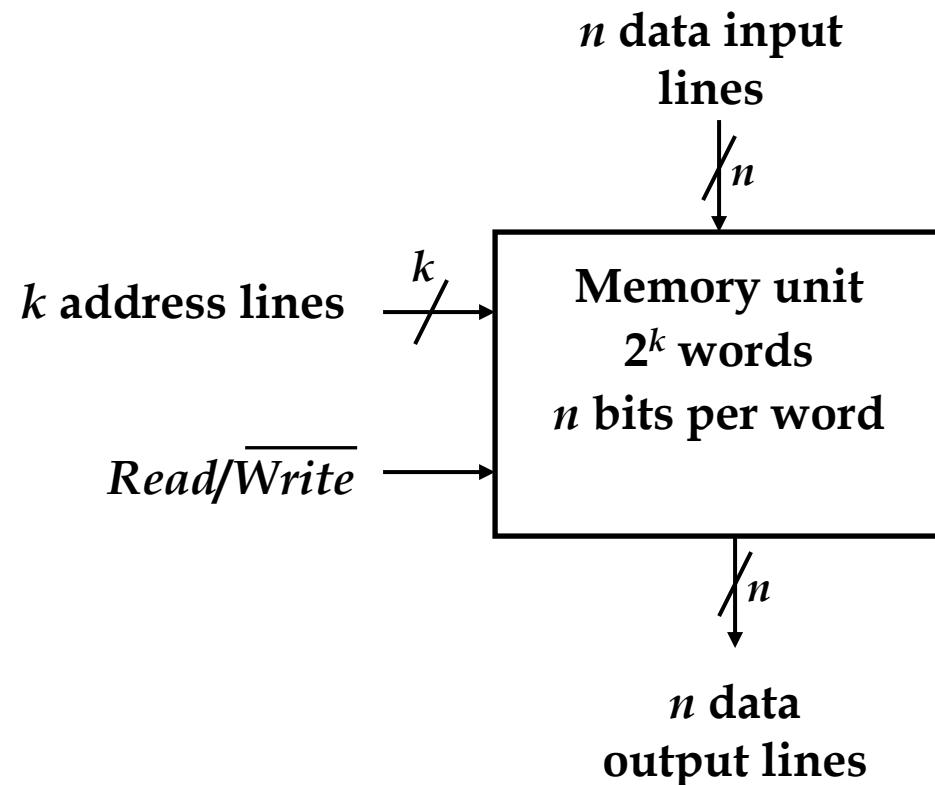


Read/Write Operations

- **Write** operation:
 - Transfers the address of the desired word to the address lines.
 - Transfers the data bits (the word) to be stored in memory to the data input lines.
 - Activates the *Write* control line (set *Read/Write* to 0).
- **Read** operation:
 - Transfers the address of the desired word to the address lines.
 - Activates the *Read* control line (set *Read/Write* to 1).


Memory Enable	<i>Read/Write</i>	Memory Operation
0	X	
1	0	
1	1	

Memory Cell

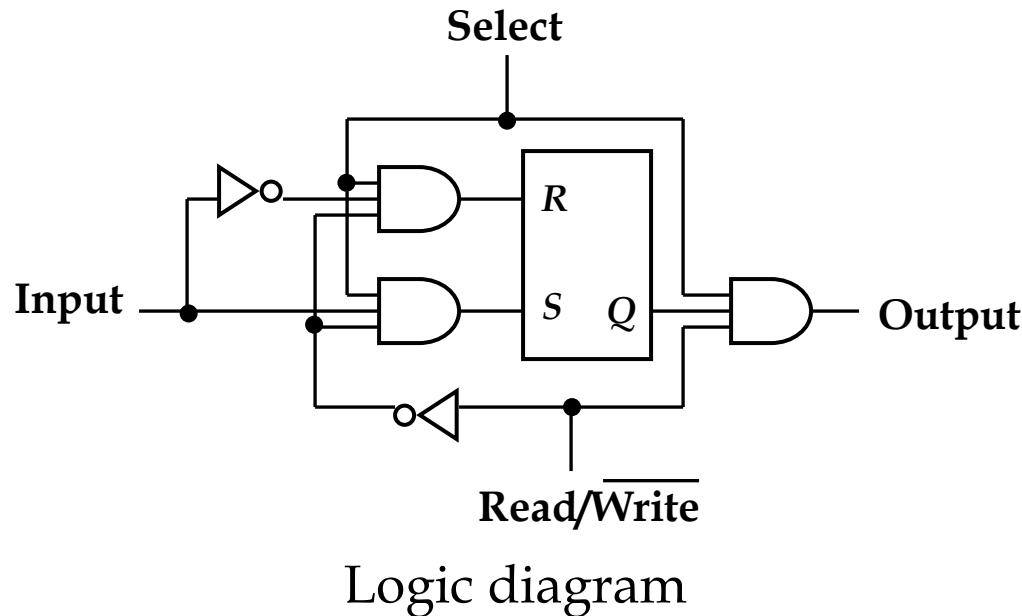- Two types of RAM
 - Static RAMs use flip-flops as the memory cells.
 - Dynamic RAMs use capacitor charges to represent data. Though simpler in circuitry, they have to be constantly refreshed.
- A single memory cell of the static RAM has the following logic and block diagrams:




Logic diagram

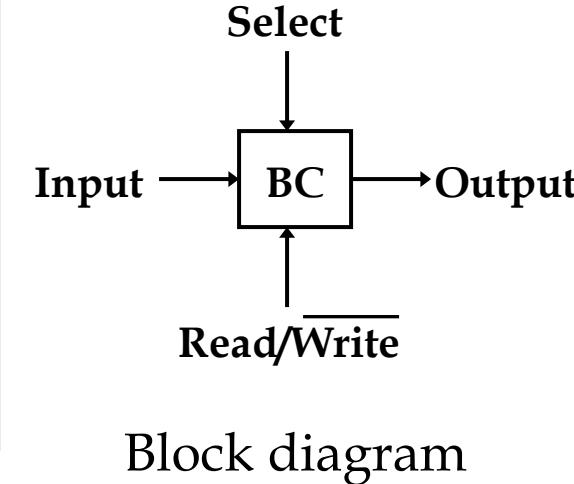

Block diagram


Memory Arrays (1/4)

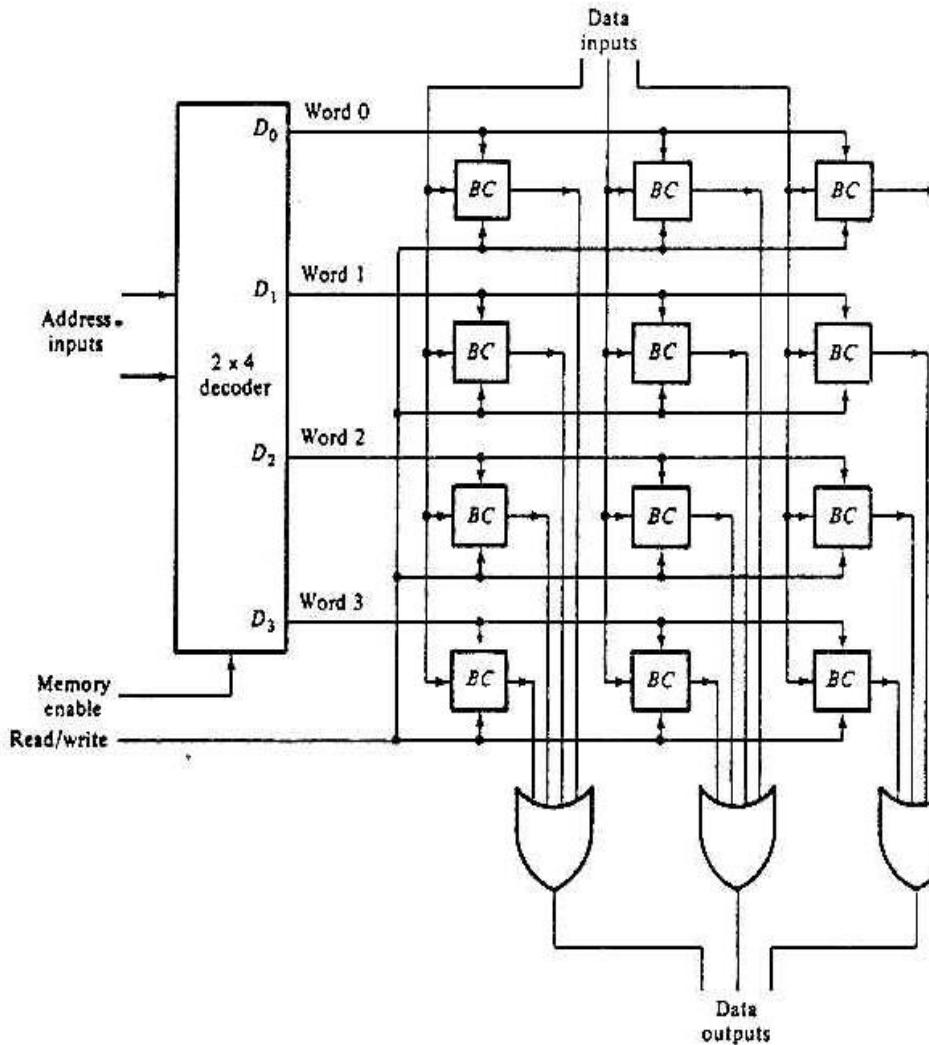- Logic construction of a 4×3 RAM (with decoder and OR gates):




Memory Arrays (2/4)

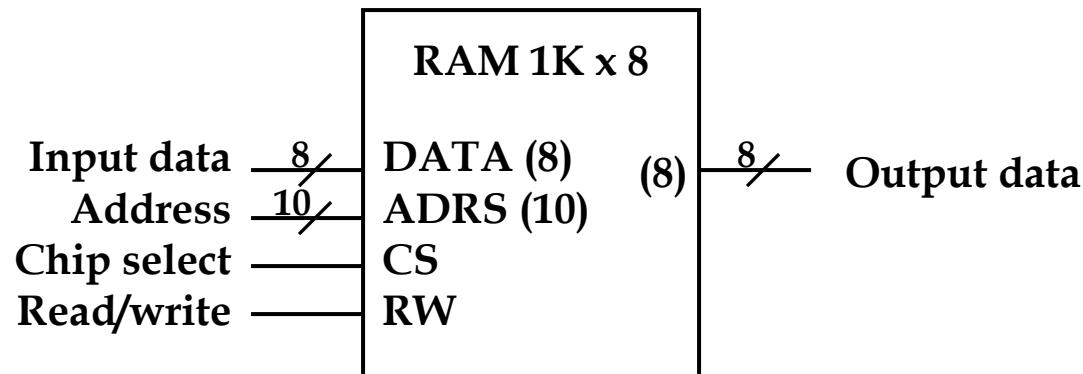- An array of RAM chips: memory chips are combined to form larger memory.
- A $1K \times 8$ -bit RAM chip:



Block diagram of a $1K \times 8$ RAM chip

Memory Arrays (3/4)

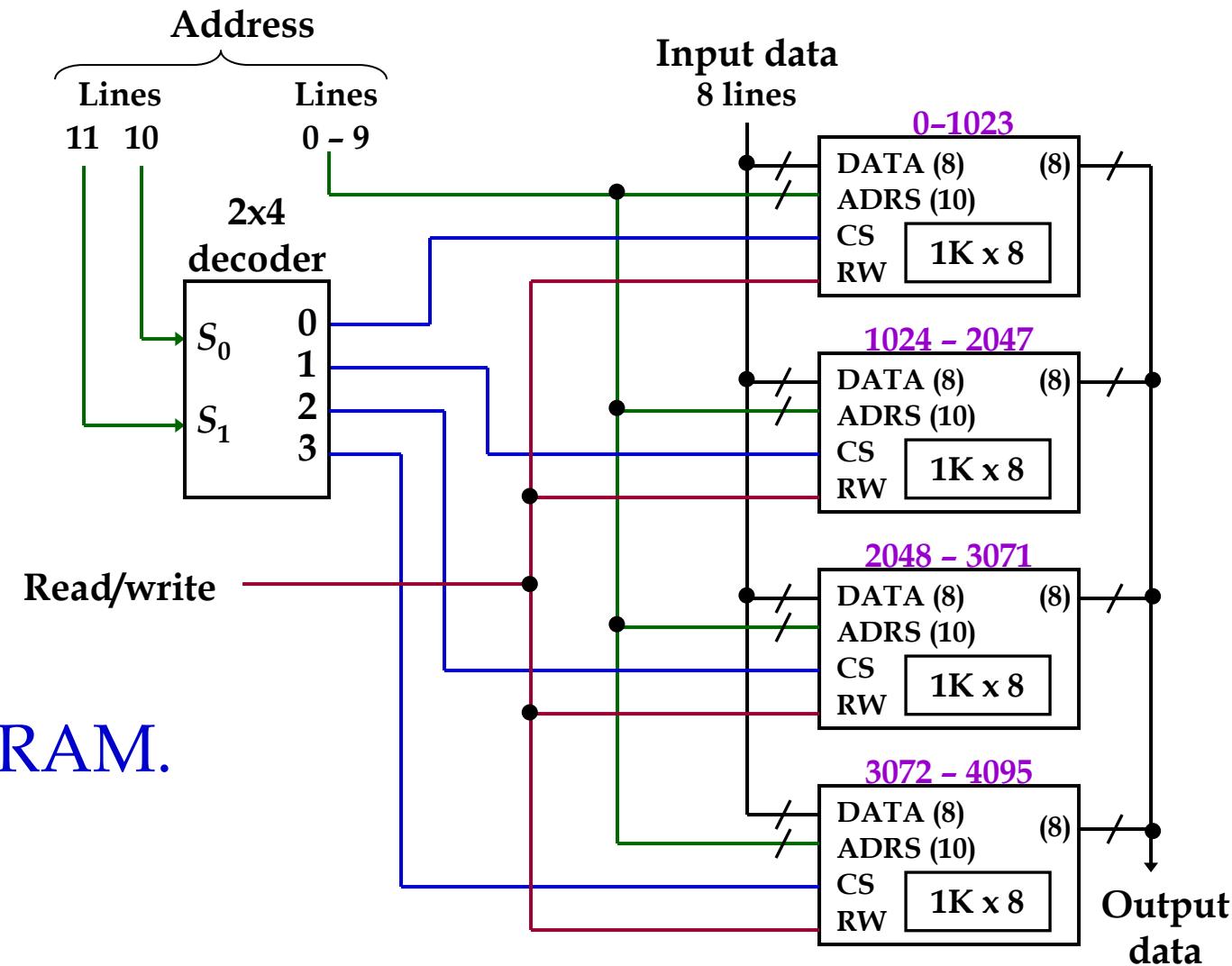

Memory Arrays (4/4)

