

Combinational Circuit: MSI (Medium Scale Integrated)

CSIM601251

Instructor: Tim Dosen DDAK

Slide By : Erdefi Rakun

Fasilkom UI




Outline

- Introduction
- Decoders
- Encoders
- Demultiplexers
- Multiplexers

Note: These slides are taken from Aaron Tan's slide

Introduction

 - Four common and useful MSI circuits:
 - Decoder
 - Demultiplexer
 - Encoder
 - Multiplexer
- Block-level outlines of MSI circuits:



Outline

- Introduction
- Decoders
- Encoders
- Demultiplexers
- Multiplexers


Note: These slides are taken from Aaron Tan's slide

Decoders (1/5)

- Codes are frequently used to represent entities, eg: your name is a code to denote yourself (an entity!).
- These codes can be identified (or decoded) using a decoder. Given a code, identify the entity.
- Convert binary information from n input lines to (maximum of) 2^n output lines.
- Known as n -to- m -line decoder, or simply $n:m$ or $n \times m$ decoder ($m \leq 2^n$).
- May be used to generate 2^n minterms of n input variables.

Decoders (2/5)

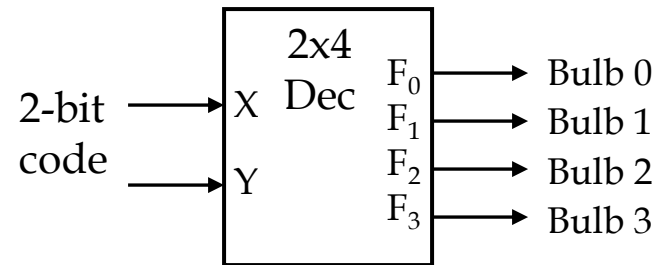- Example: If codes 00, 01, 10, 11 are used to identify four light bulbs, we may use a 2-bit decoder.



- This is a **2×4 decoder** which selects an output line based on the 2-bit code supplied.
- Truth table:


X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Decoders (3/5)

- From truth table, circuit for **2×4 decoder** is:

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 
- Note: Each output is a 2-variable minterm (**$X' \cdot Y'$** , **$X' \cdot Y$** , **$X \cdot Y'$** or **$X \cdot Y$**)



Decoders (4/5)


- Design a 3×8 decoder.

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

Decoders (5/5)

 - In general, for an n -bit code, a decoder could select up to 2^n lines:



Decoders: Implementing Functions (1/5)

- A Boolean function, in sum-of-minterms form a decoder to generate the minterms, and an OR gate to form the sum.
- Any combinational circuit with n inputs and m outputs can be implemented with an $n:2^n$ decoder with m OR gates.
- Good when circuit has many outputs, and each function is expressed with few minterms.


Decoders: Implementing Functions (2/5)

- Example: Full adder


$$S(x, y, z) = \sum m(1,2,4,7)$$

$$C(x, y, z) = \sum m(3,5,6,7)$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Decoders: Implementing Functions (3/5)

 


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Decoders: Implementing Functions (4/5)

 

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Decoders: Implementing Functions (5/5)

 

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Decoders with Enable (1/2)

- Decoders often come with an *enable* control signal, so that the device is only activated when the enable, $E = 1$.

- Truth table:

E	X	Y	F ₀	F ₁	F ₂	F ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	X	X	0	0	0	0

 - Circuit of a **2×4 decoder with enable**:



Decoders with Enable (2/2)

- In the previous slide, the decoder has a **one-enable** control signal, i.e. the decoder is enabled with $E=1$.
- In most MSI decoders, enable signal is **zero-enable**, usually denoted by E' or $\bar{E}$. The decoder is enabled when the signal is zero (low).

E	X	Y	F ₀	F ₁	F ₂	F ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	X	X	0	0	0	0



Decoder with 1-enable

E'	X	Y	F ₀	F ₁	F ₂	F ₃
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	X	X	0	0	0	0



Decoder with 0-enable

Larger Decoders (1/3)

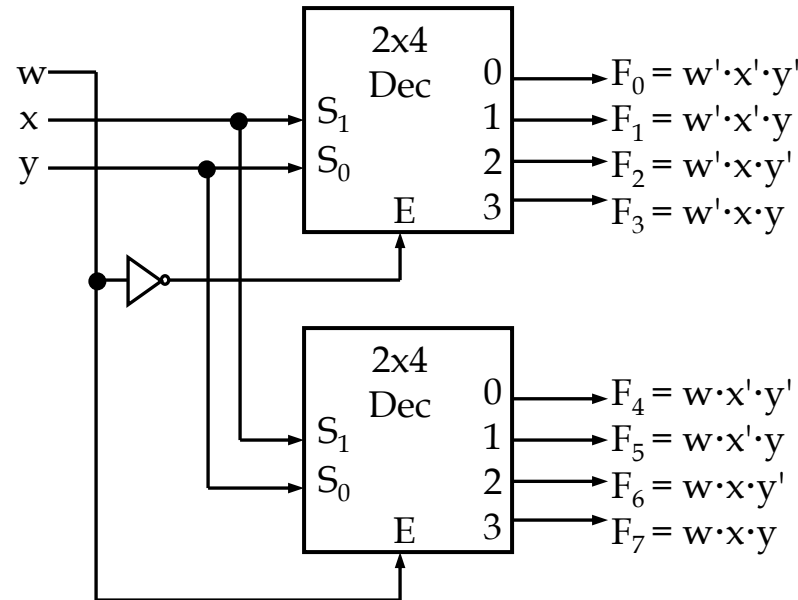 - Larger decoders can be constructed from smaller ones.
- Example: A 3×8 decoder can be built from two 2×4 decoders (with one-enable) and an inverter.





Larger Decoders (2/3)

  

Larger Decoders (3/3)

  - Construct a 4×16 decoder from two 3×8 decoders with one enable.




Outline

- Introduction
- Decoders
- Encoders
- Demultiplexers
- Multiplexers

Note: These slides are taken from Aaron Tan's slide

Encoders (1/4)

 - **Encoding** is the converse of decoding.
- Given a set of input lines, of which exactly one is high, the **encoder** provides a code that corresponds to that input line.
- Contains 2^n (or fewer) input lines and n output lines.
- Implemented with OR gates.
- Example:



Encoders (2/4)

- Truth table:
- With K-map, we obtain:
 $D_0 = F_1 + F_3$
 $D_1 = F_2 + F_3$
- Circuit:

F_0	F_1	F_2	F_3	D_1	D_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1
0	0	0	0	X	X
0	0	1	1	X	X
0	1	0	1	X	X
0	1	1	0	X	X
0	1	1	1	X	X
1	0	0	1	X	X
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X


Encoders (3/4)

- Example: Octal-to-binary encoder.
 - At any one time, only one input line has a value of 1.
 - Otherwise, we need **priority encoder**.

Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Encoders (4/4)

- Example: Octal-to-binary encoder.

 

An 8-to-3 encoder

- Exercise: Can you design a 2^n -to- n encoder without using K-map?


Outline

- Introduction
- Decoders
- Encoders
- Demultiplexers
- Multiplexers

Note: These slides are taken from Aaron Tan's slide


Demultiplexers (1/2)

 - Given an input line and a set of selection lines, a **demultiplexer** directs data from the input to one selected output line.
- Example: **1-to-4 demultiplexer**.



Demultiplexers (2/2)

 - It turns out that the demultiplexer circuit is actually identical to a decoder with enable.




Outline

- Introduction
- Decoders
- Encoders
- Demultiplexers
- Multiplexers

Note: These slides are taken from Aaron Tan's slide

Multiplexers (1/5)

 - A **multiplexer** is a device which has
 - A number of input lines
 - A number of selection lines
 - One output line
- It steers one of 2^n inputs to a single output line, using n selection lines. Also known as a *data selector*.





Multiplexers (2/5)

- Truth table for a 4-to-1 multiplexer:

I_0	I_1	I_2	I_3	S_1	S_0	Y
d_0	d_1	d_2	d_3	0	0	d_0
d_0	d_1	d_2	d_3	0	1	d_1
d_0	d_1	d_2	d_3	1	0	d_2
d_0	d_1	d_2	d_3	1	1	d_3

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

  

Multiplexers (3/5)

- Output of multiplexer is
“sum of the (product of *data lines* and *selection lines*)”
- Example: Output of a 4-to-1 multiplexer is:



S ₁	S ₀	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

$$Y = I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$

- A 2^n -to-1-line multiplexer, or simply $2^n:1$ MUX, is made from an $n:2^n$ decoder by adding to it 2^n input lines, one to each AND gate.


Multiplexers (4/5)

- A 4:1 multiplexer circuit:

  

Multiplexers (5/5)


- An application:

 

- Helps share a *single communication line* among a number of devices.
- At any time, only one source and one destination can use the communication line.


Larger Multiplexers (1/4)

 - Larger multiplexers can be constructed from smaller ones.
- An 8-to-1 multiplexer can be constructed from smaller multiplexers like this (note placement of selector lines):



S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇


Larger Multiplexers (2/4)

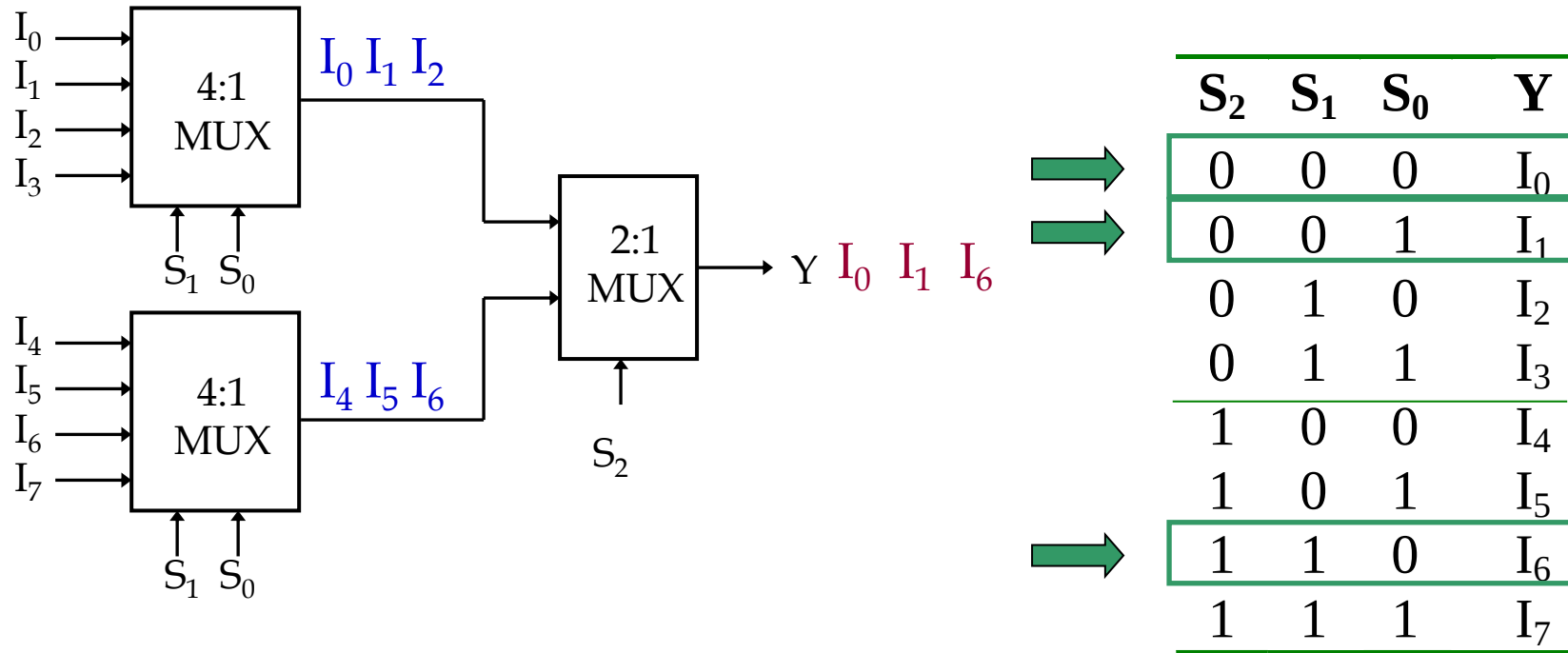

- When $S_2S_1S_0 = 000$
- When $S_2S_1S_0 = 001$
- When $S_2S_1S_0 = 110$

Larger Multiplexers (3/4)

 - Another implementation of an 8-to-1 multiplexer using smaller multiplexers:




S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Q: Can we use only 2:1 multiplexers?

Larger Multiplexers (4/4)

 - A 16-to-1 multiplexer can be constructed from five 4-to-1 multiplexers:




Multiplexers: Implementing Functions (1/3)

- Boolean functions can be implemented using multiplexers.
- A 2^n -to-1 multiplexer can implement a Boolean function of n input variables, as follows:
 1. Express in sum-of-minterms form. Example:
$$F(A,B,C) = A' \cdot B' \cdot C + A' \cdot B \cdot C + A \cdot B' \cdot C + A \cdot B \cdot C'$$
$$= \sum m(1,3,5,6)$$
 2. Connect n variables to the n selection lines.
 3. Put a '1' on a data line if it is a minterm of the function, or '0' otherwise.

Multiplexers: Implementing Functions (2/3)

- $F(A,B,C) = \sum m(1,3,5,6)$

 

This method works because:

$$\text{Output} = m_0 \cdot I_0 + m_1 \cdot I_1 + m_2 \cdot I_2 + m_3 \cdot I_3 \\ + m_4 \cdot I_4 + m_5 \cdot I_5 + m_6 \cdot I_6 + m_7 \cdot I_7$$

Supplying '1' to I_1, I_3, I_5, I_6 , and '0' to the rest:

$$\text{Output} = m_1 + m_3 + m_5 + m_6$$

Multiplexers: Implementing Functions (3/3)

- Example: Use a 74151A to implement $f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$


i	C	B	A	Y
	x_1	x_2	x_3	f
0	0	0	0	1 $D_0 = 1$
1	0	0	1	0 $D_1 = 0$
2	0	1	0	1 $D_2 = 1$
3	0	1	1	1 $D_3 = 1$
4	1	0	0	0 $D_4 = 0$
5	1	0	1	1 $D_5 = 1$
6	1	1	0	0 $D_6 = 0$
7	1	1	1	0 $D_7 = 0$

(a)


Realization of $f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$.

(a) Truth table.

(b) Implementation with 74151A.

 

Peeking Ahead (1/2)

 

Peeking Ahead (2/2)

